




# MICROPHONE PHASE DETECTOR AND INDICATOR

Parker Foresman

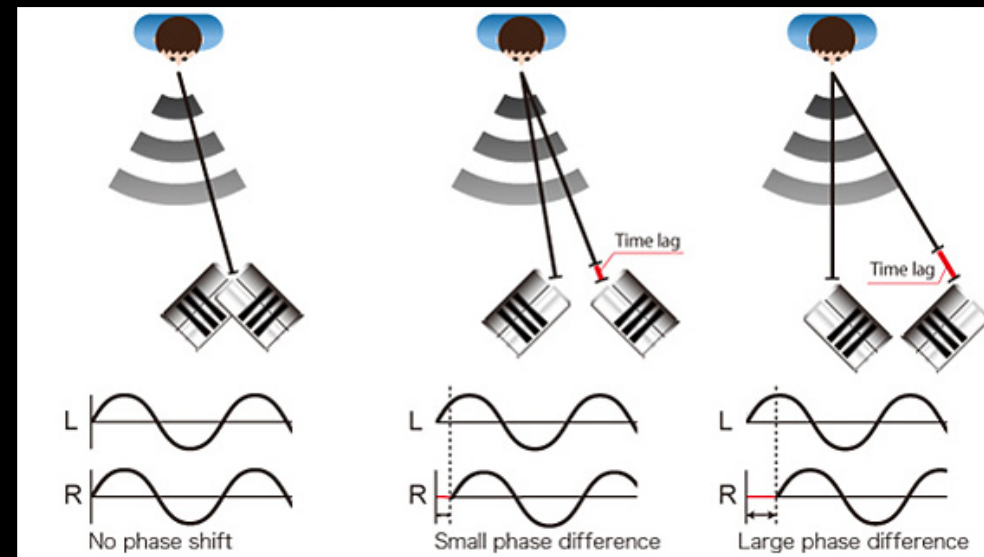
# PHASE IN CONTEXT

- Defined as the **time delay** of a given signal from a reference signal
- Microphones at varying distances from a common source result in differences in signal phase
  - Due to slight time lag


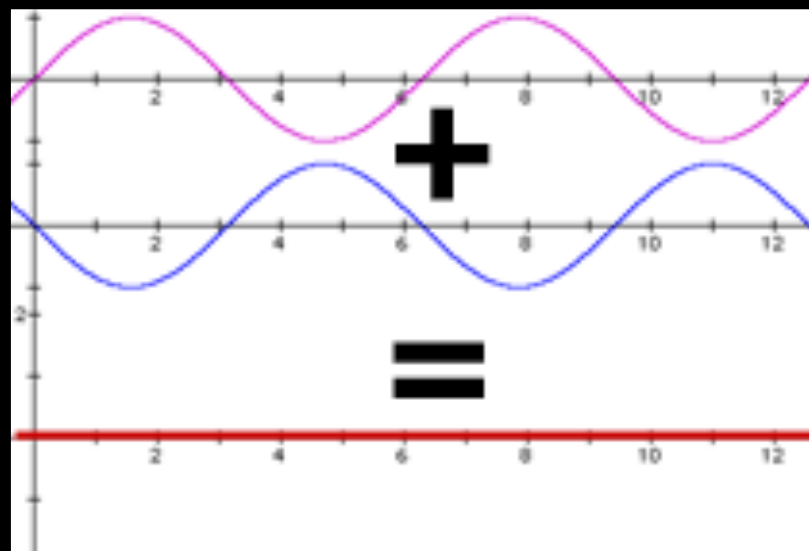
# THE PROBLEM

- When recording using multiple microphones, "out of phase" signals can cause phase cancellations
  - Positive and negative portions of the waveform cancel each other out
  - e.g. 400Hz sinusoid recorded by microphones about 1.5' apart
- Phase cancellations between microphones can cause dull sounding recordings



# GOALS

- Accurately detect the phase of multiple microphone signals relative to a reference microphone
- Indicate any “out of phase” signals to the user
- Would allow for an optimized multi-microphone setup
  - Minimum phase cancellation between microphones
  - Better quality recordings or live mix
- Would be used by amateur or professional audio engineers to help achieve full sounding recordings




# PERFORMANCE CRITERIA

- Detect phase difference with less than 5% error
- Indicate the magnitude of phase difference between inputs
- Indicate all phase differences with a turnaround time of less than 20 seconds
- At least 5 XLR inputs
- Powered by line voltage w/transformer
  - 12V DC
- Less than \$300
  - To allow for amateur use
- Around 8"W x 6"D x 2"H
  - Small enough to easily transport
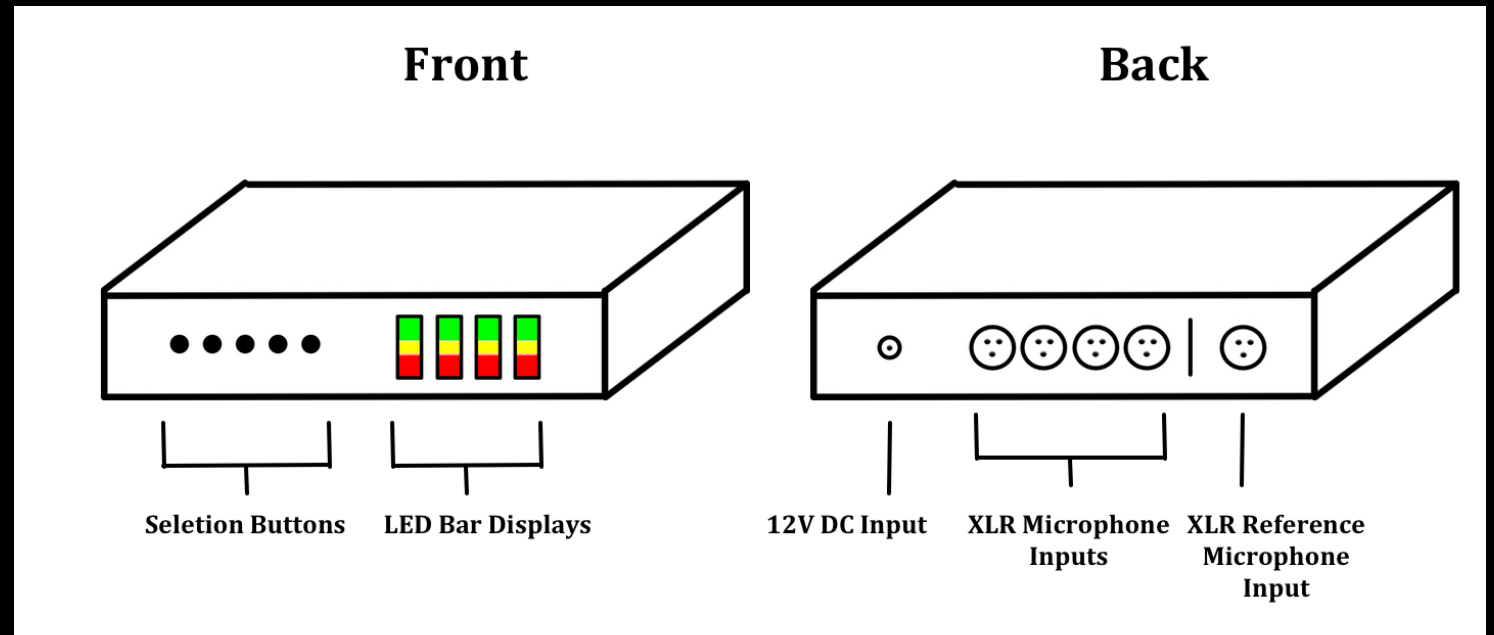
# IMPLEMENTATION




- 5 XLR inputs and 5 microphone preamplifiers
  - One reference input
- 4 phase correlation circuits
- 4 LED bar display indicators
- ON and selection Buttons




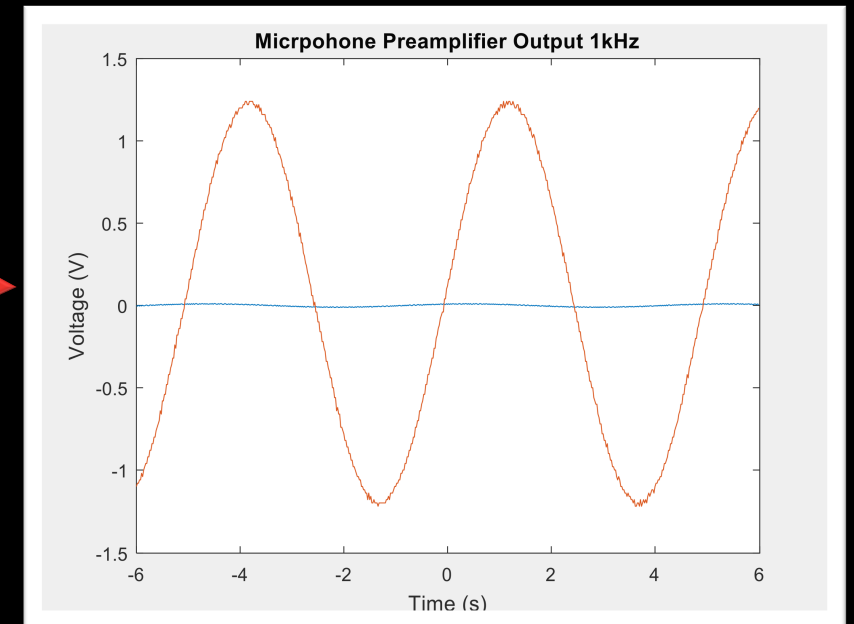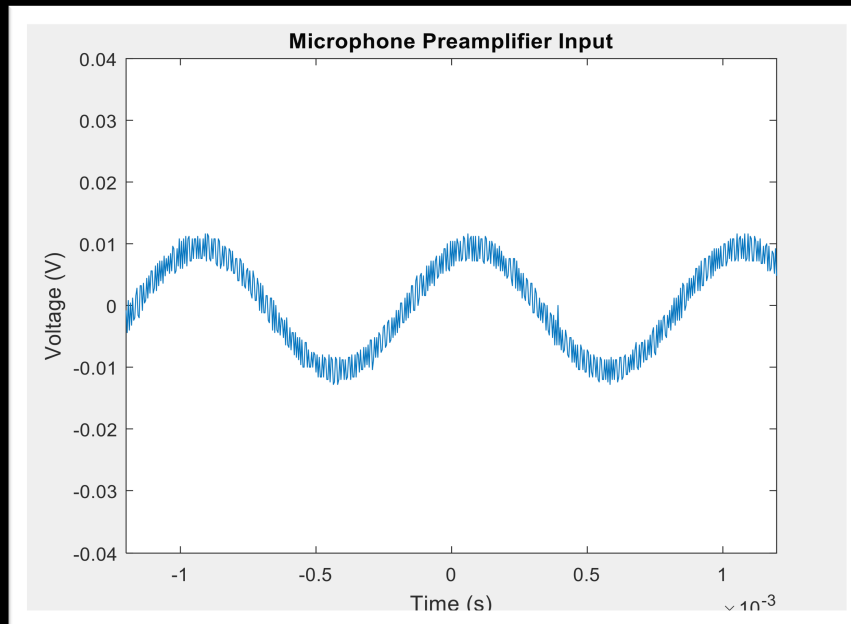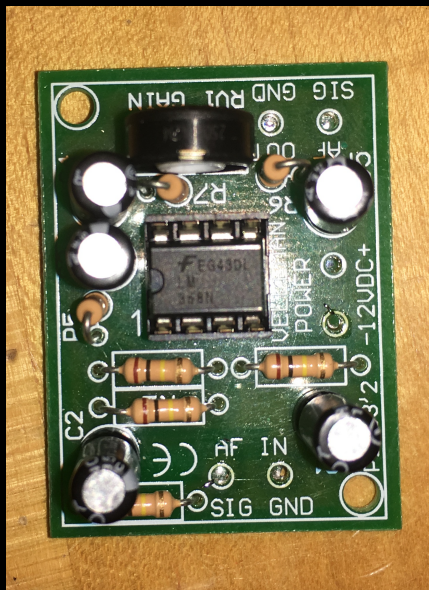
# PREAMPLIFICATION


- To raise small microphone voltage level for proper reading
- Velleman K1803 Preamplifier Kit





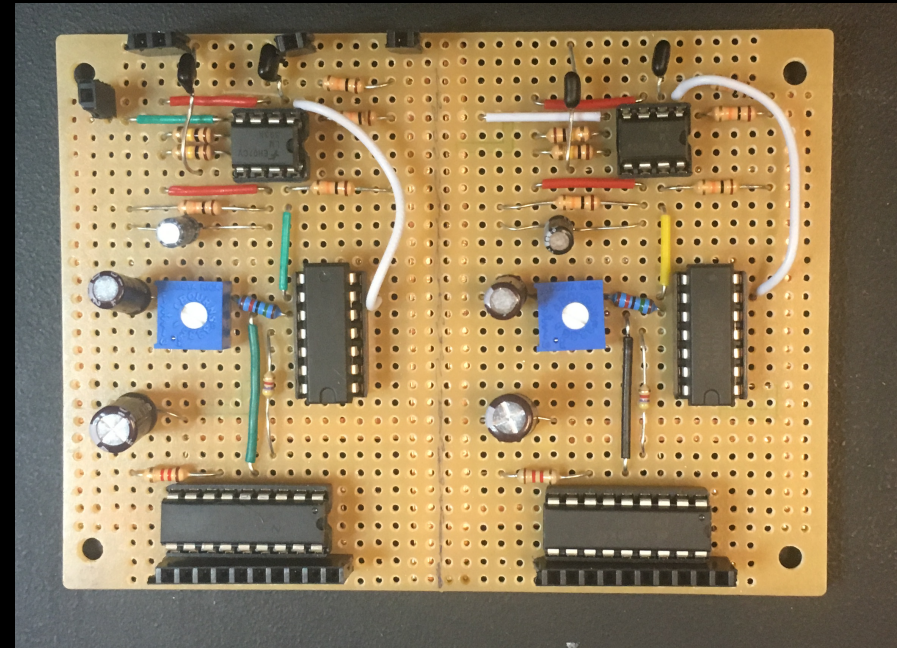
# PHASE CORRELATION CIRCUIT

- Adjusts output voltage relative to phase difference between input signals
- Uses high gain clipping amplifiers, XOR gates, and a low pass filter
- Output voltage is sent to an LED controller





# Schematic


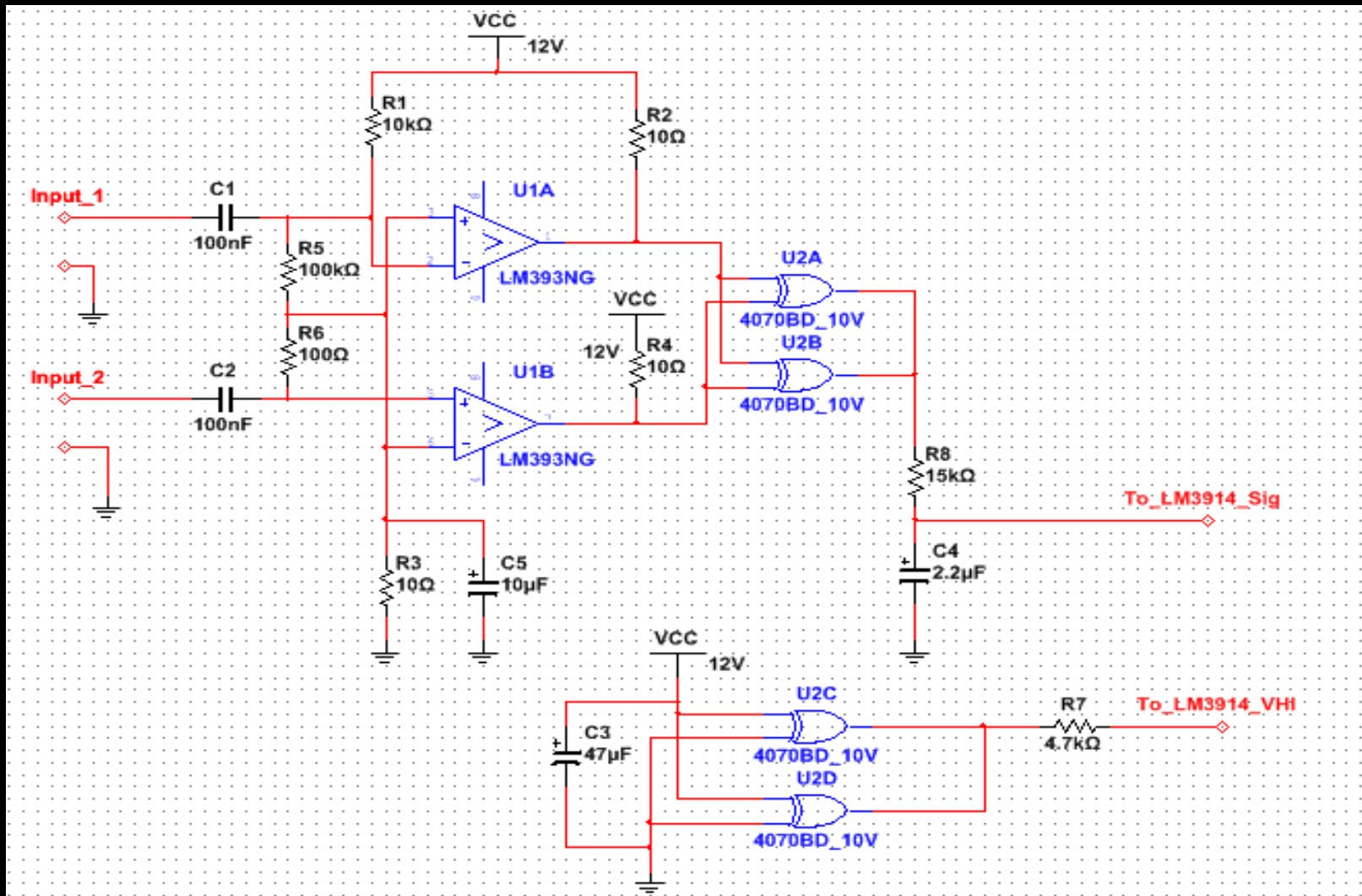





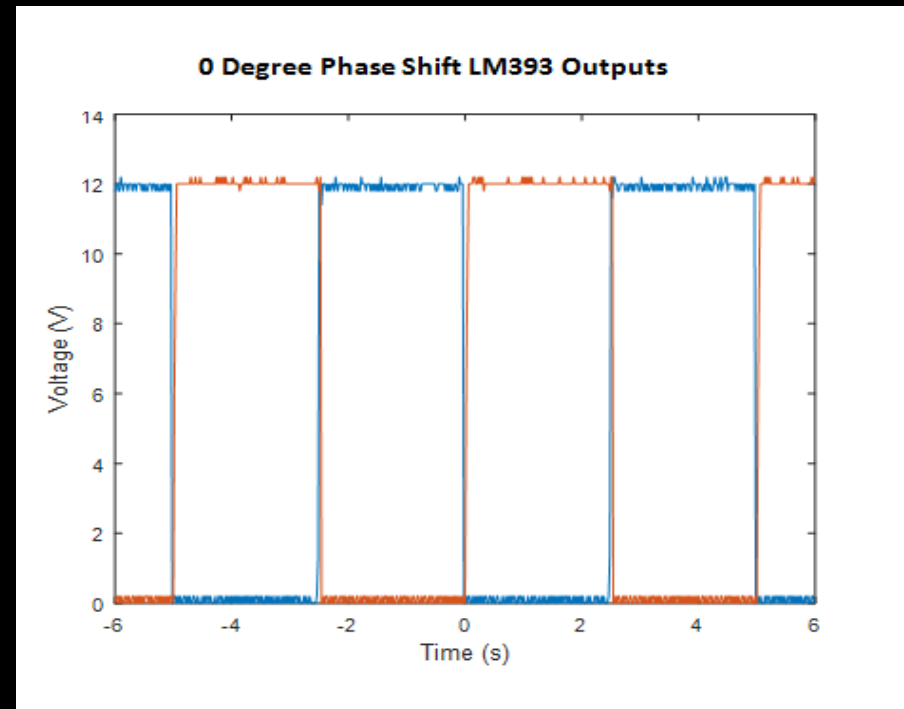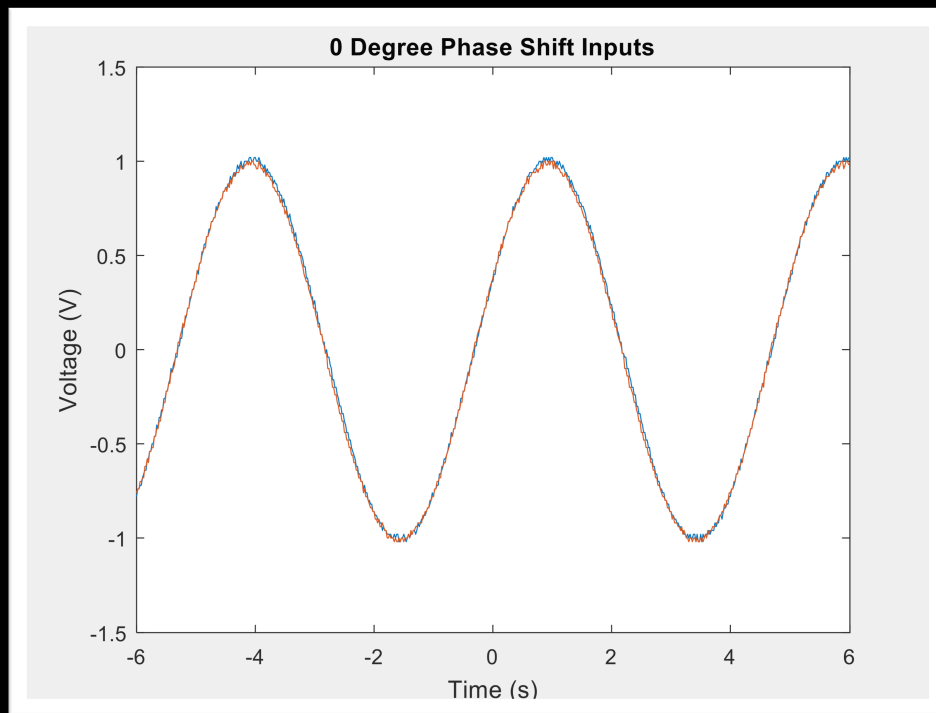
# HIGH GAIN CLIPPING AMPLIFIER

- Turns input signals into square waves of equal amplitude
  - Note: one amplifier is inverted





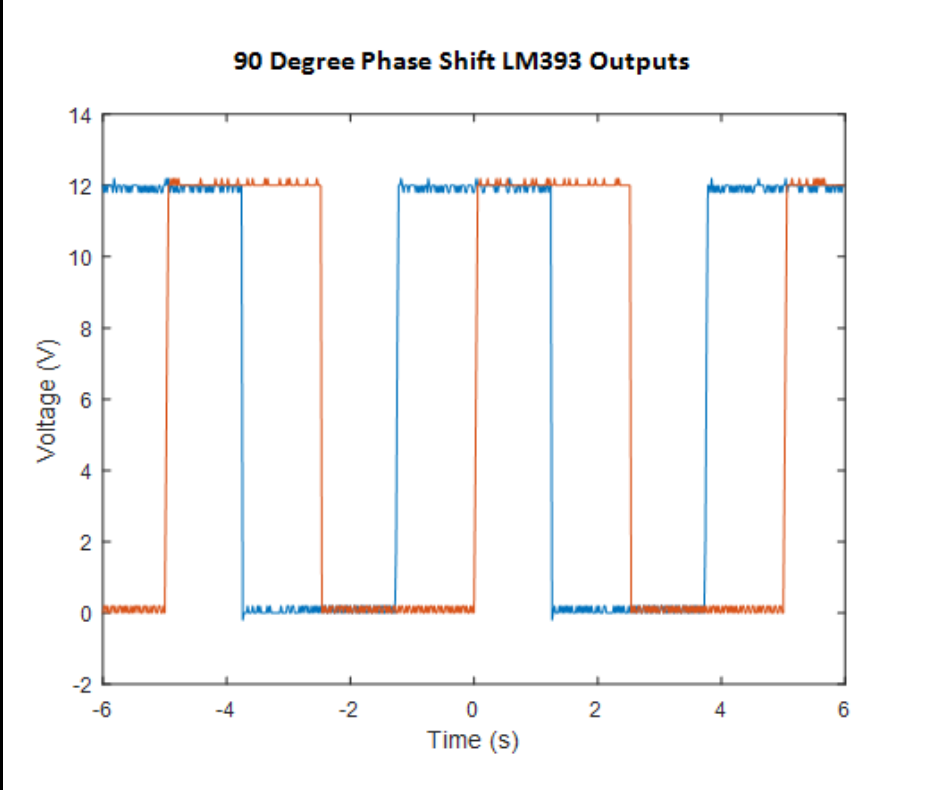
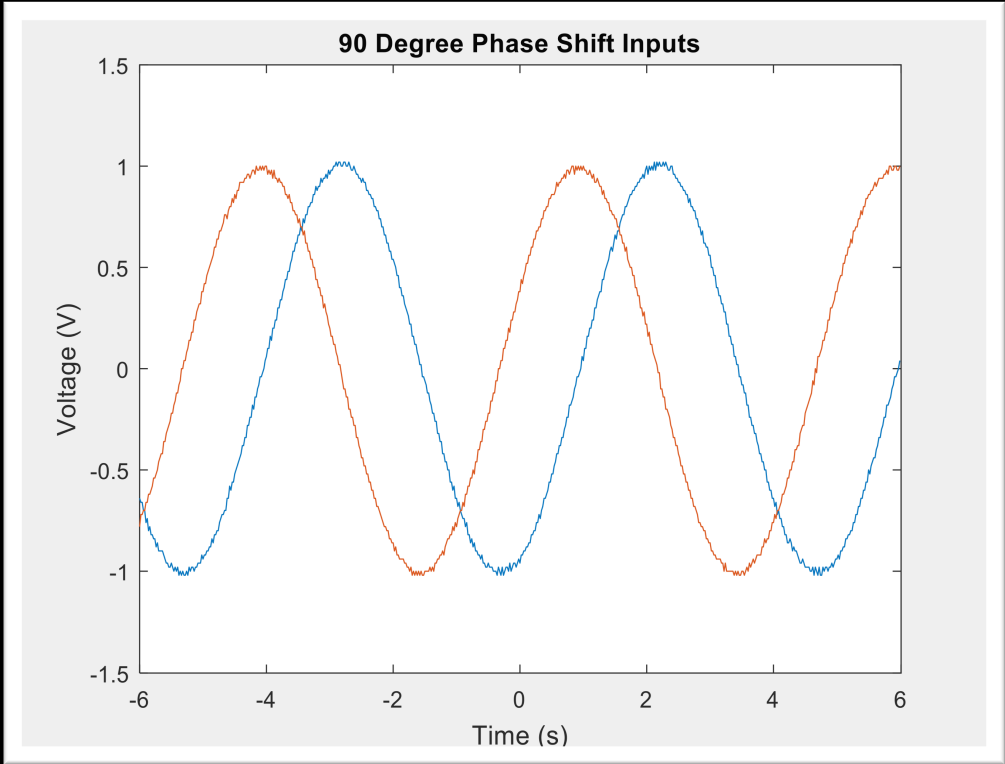


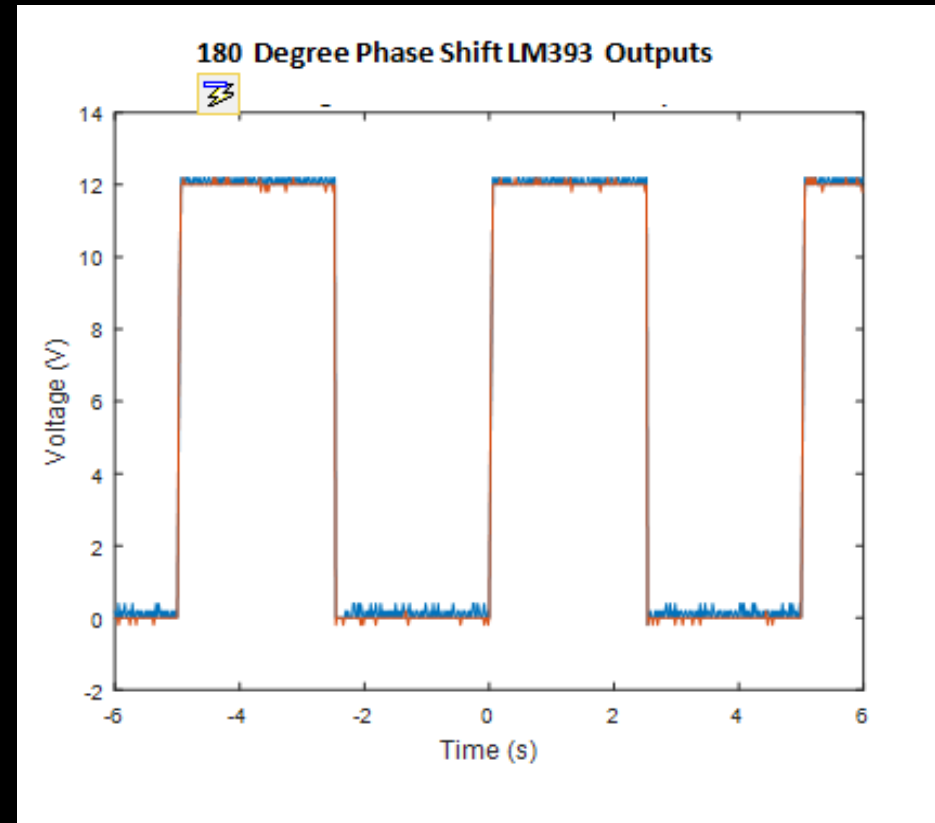
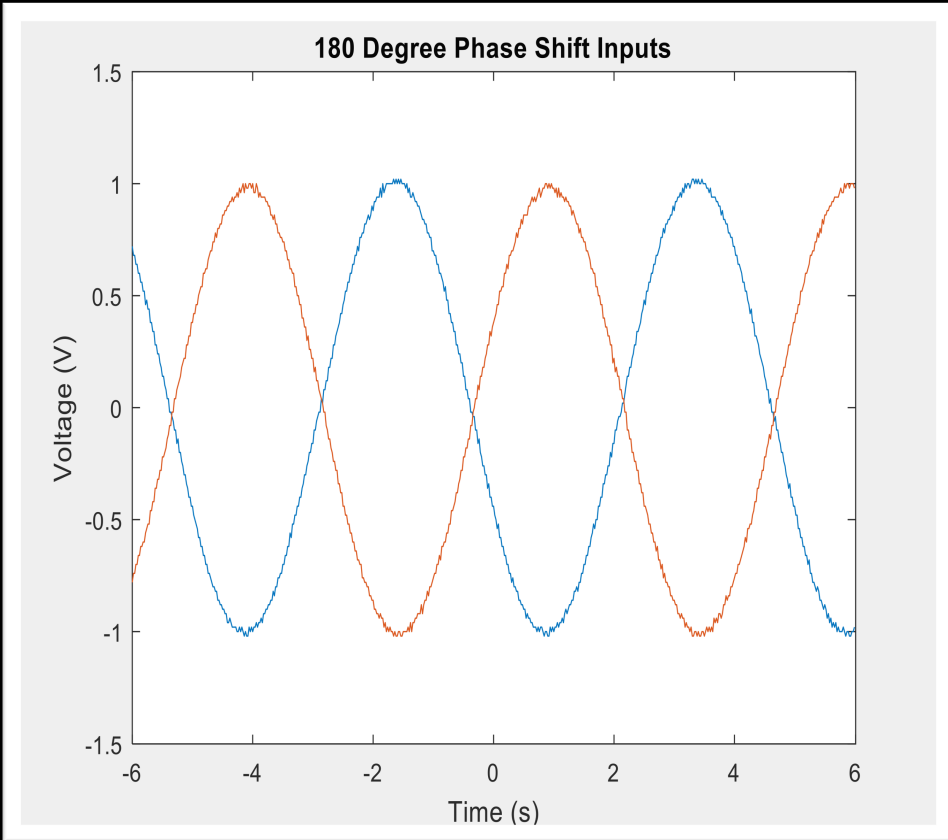

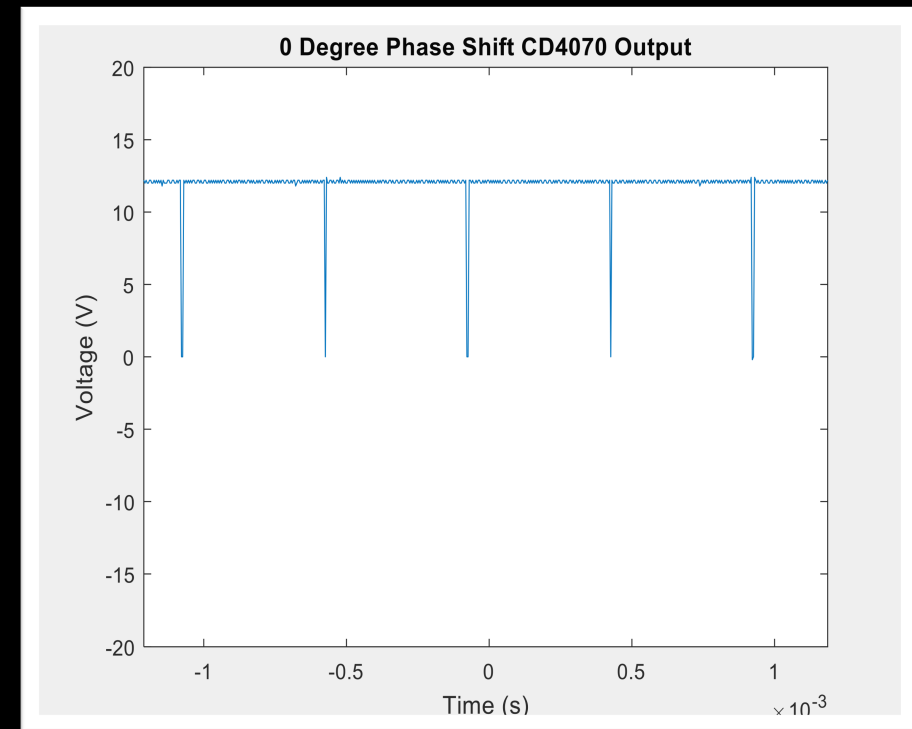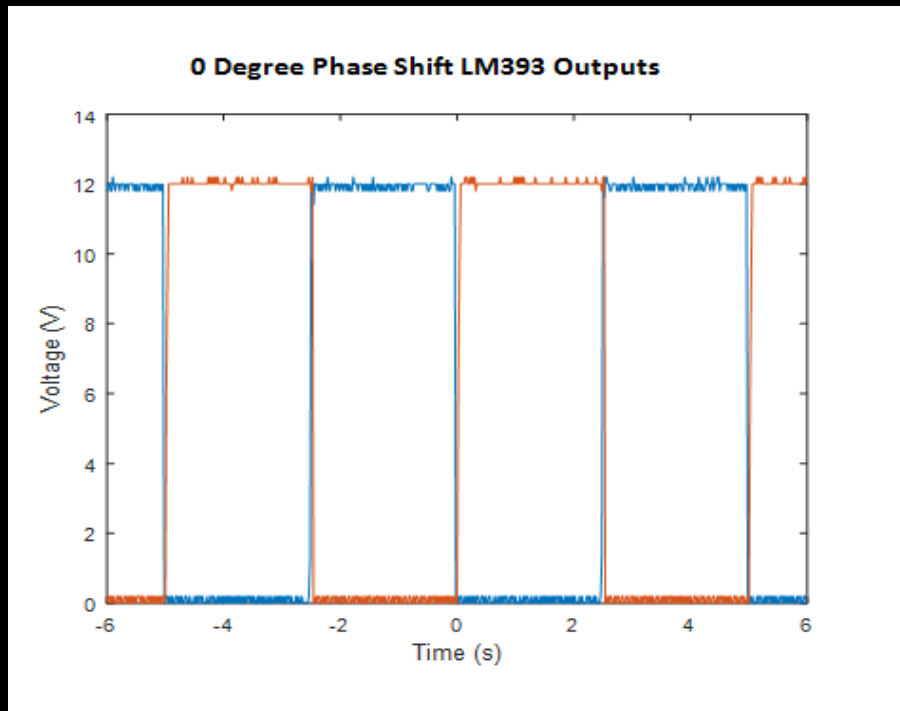
# XOR GATE

- Takes the XOR of both signals and outputs a single voltage



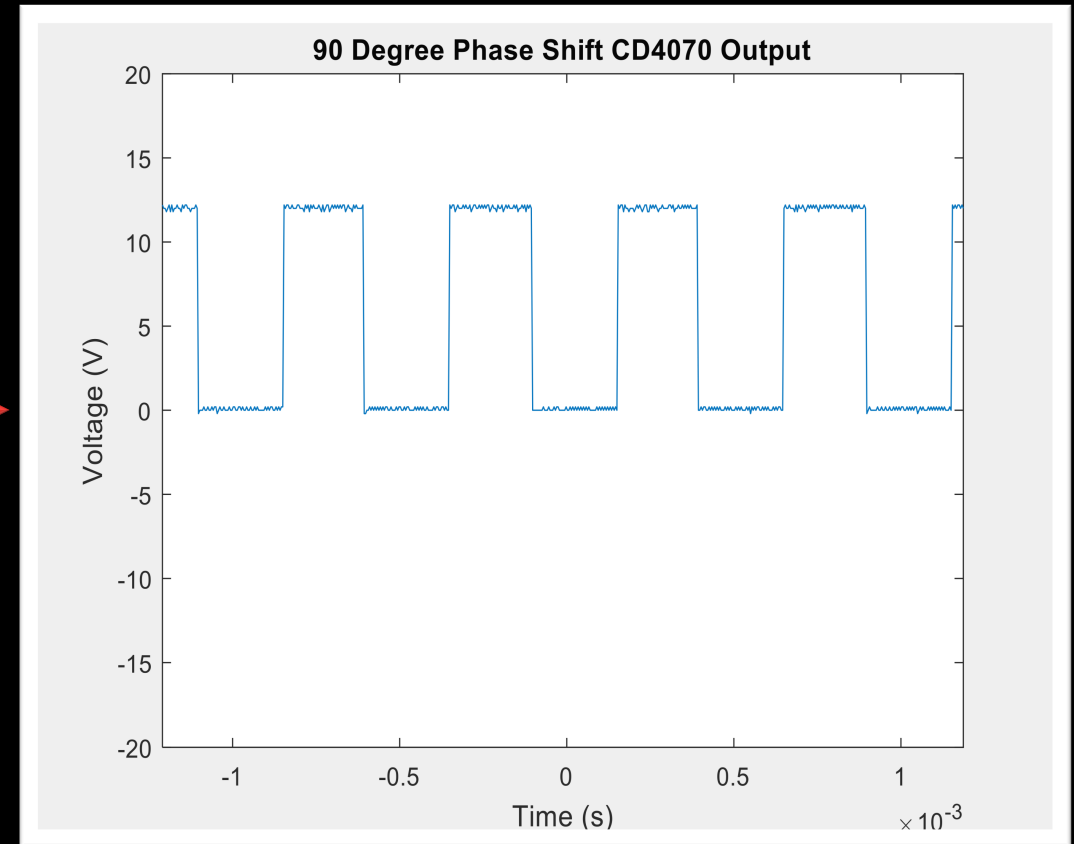
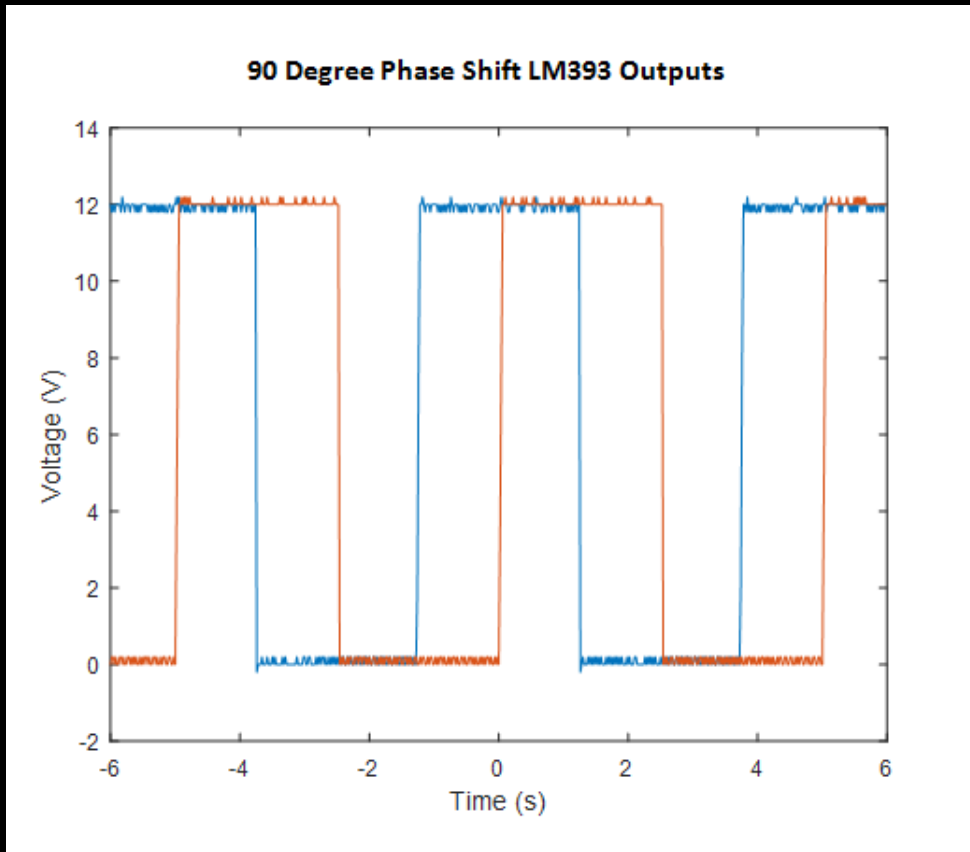


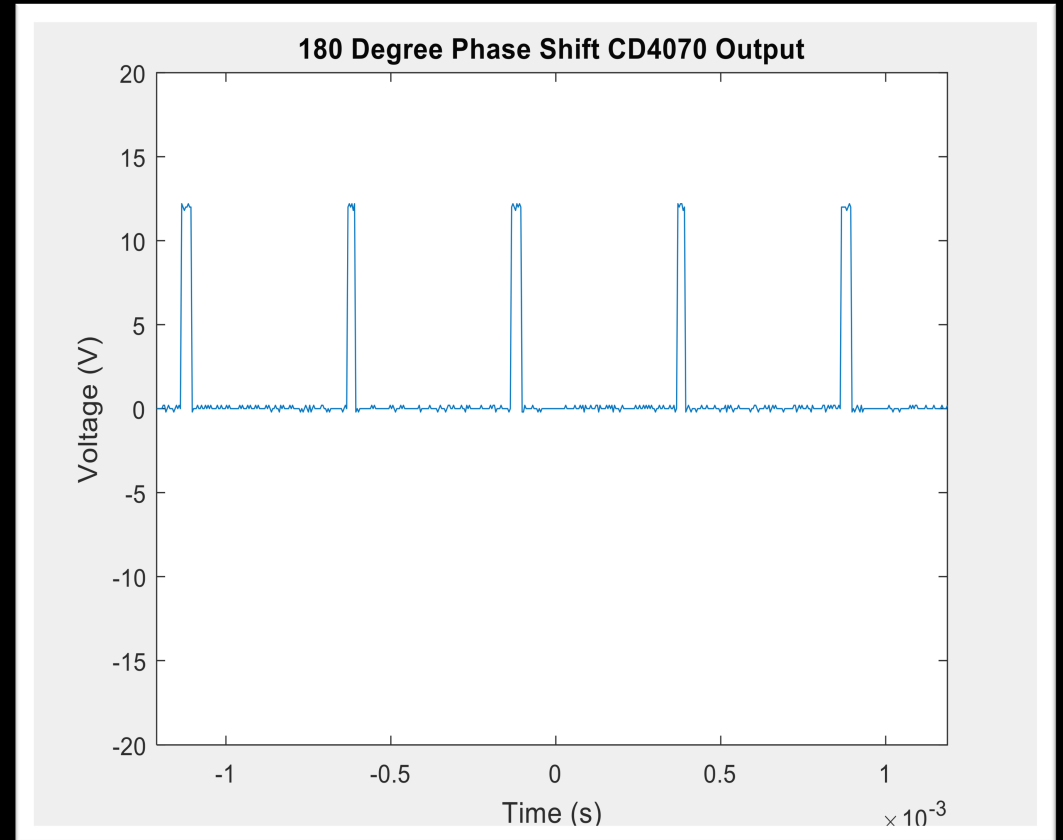
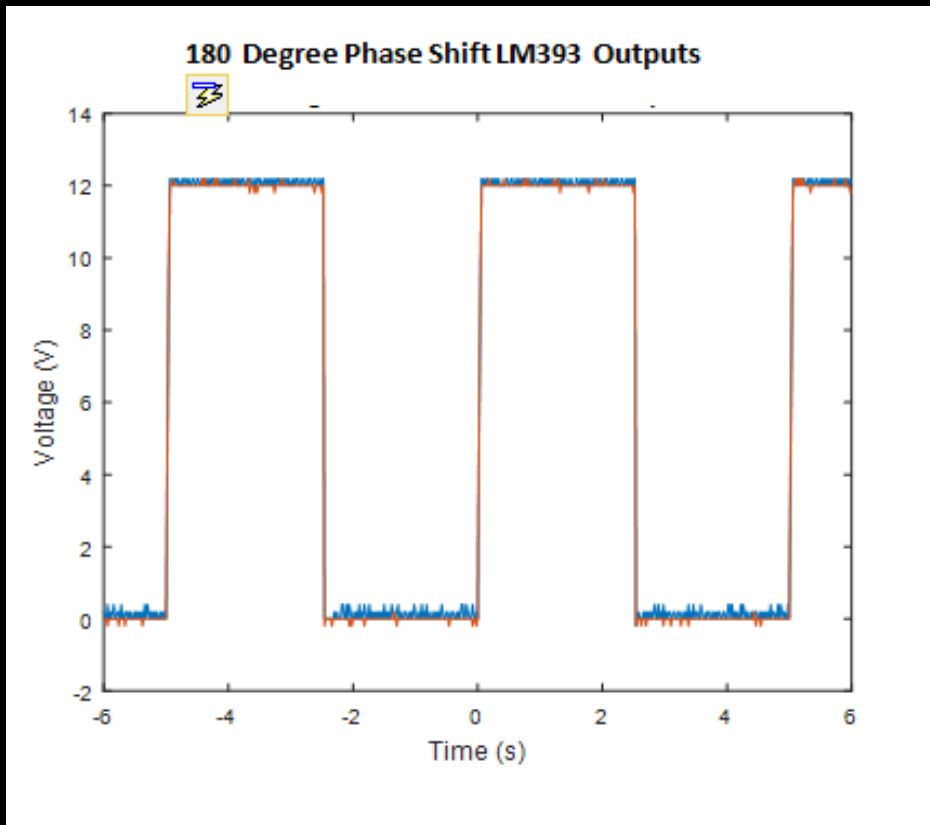





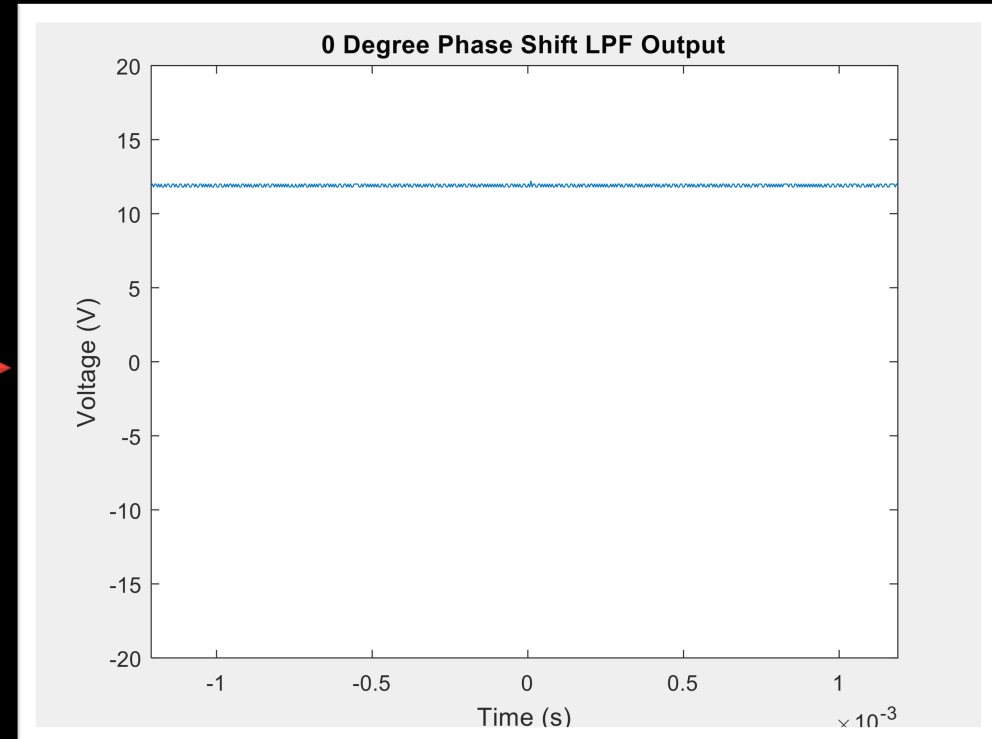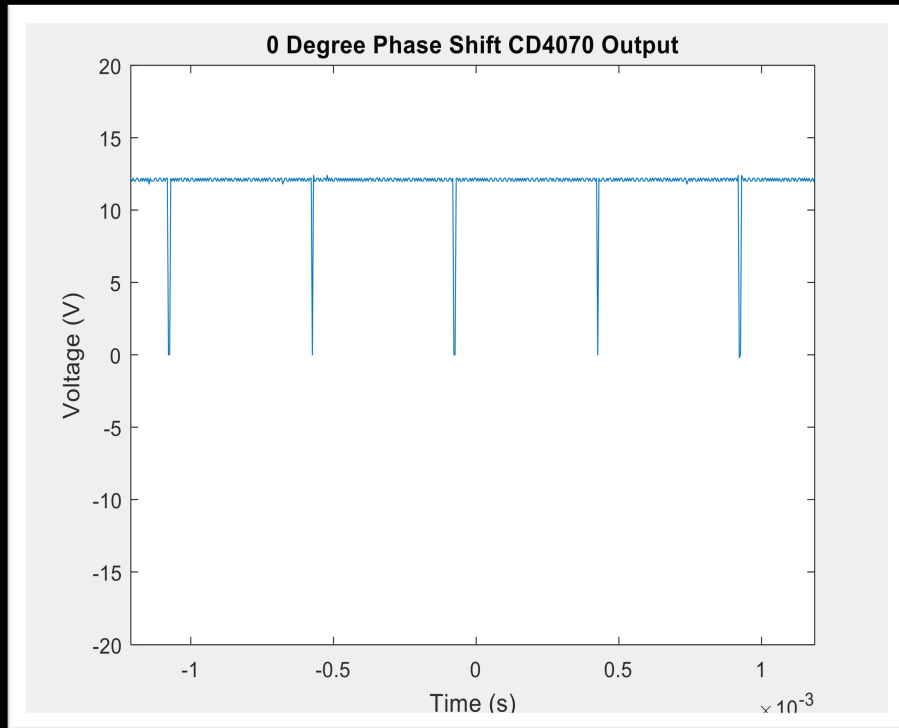
# LOW PASS FILTER

- Reduces high frequency components and acts as a moving averager



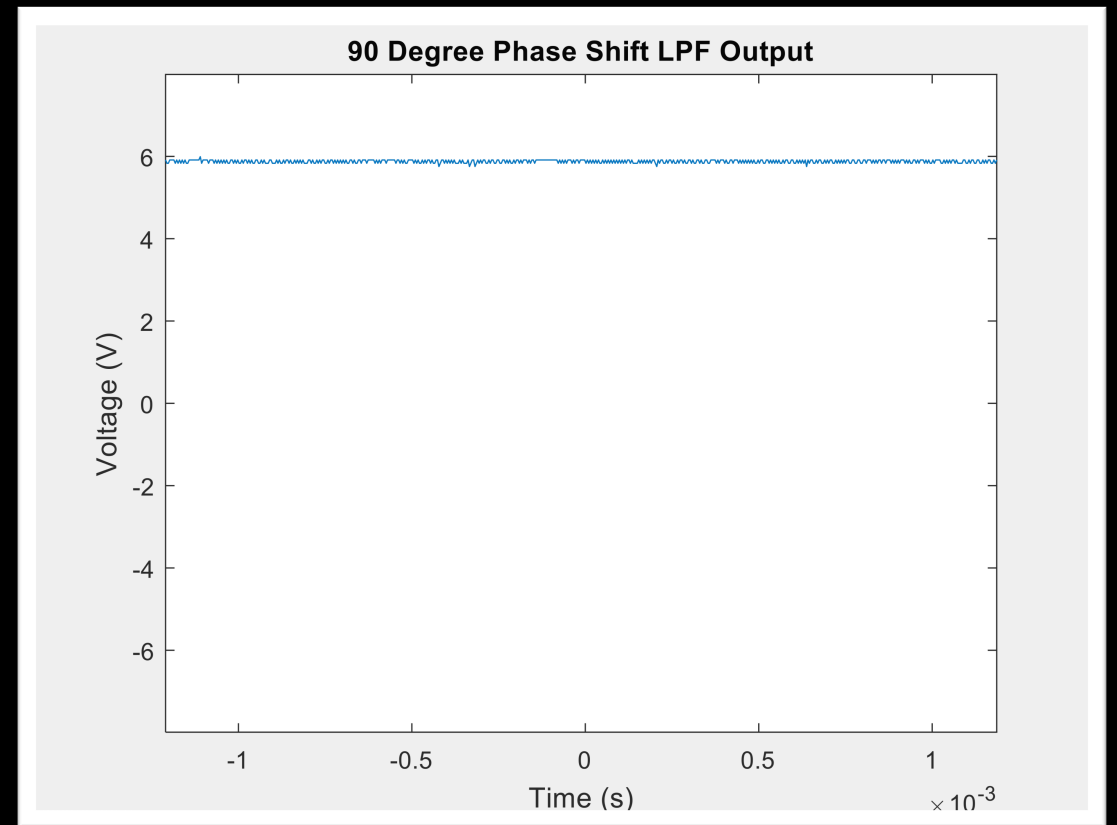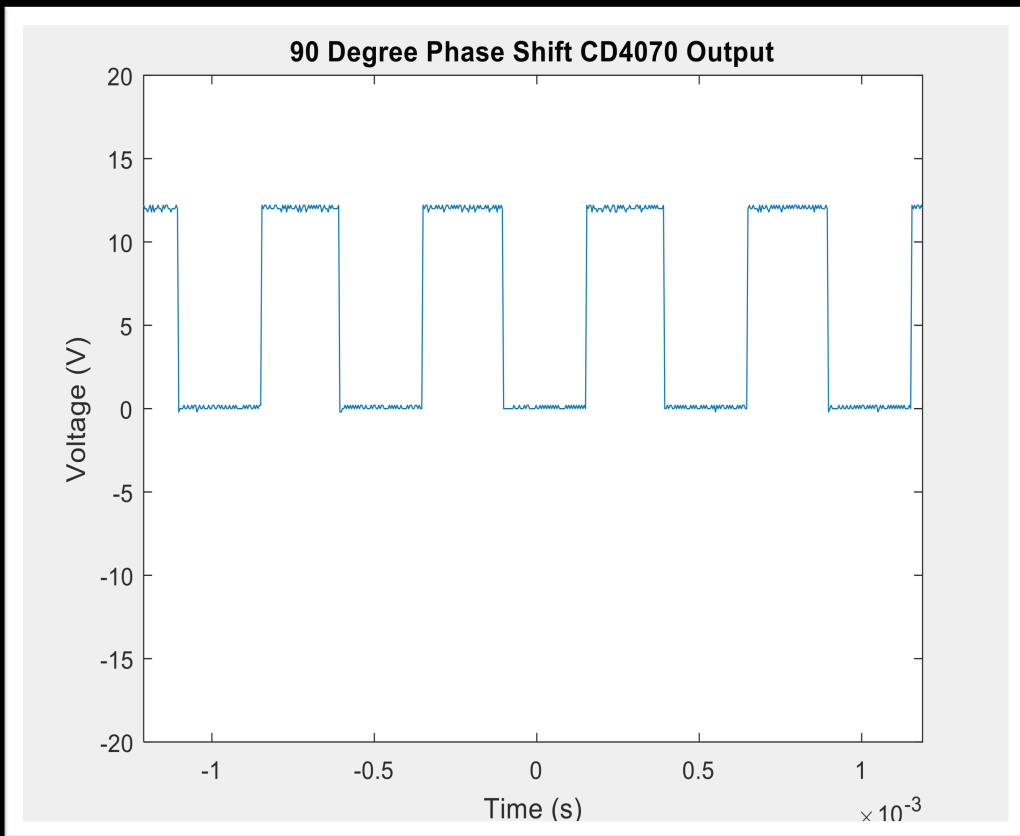

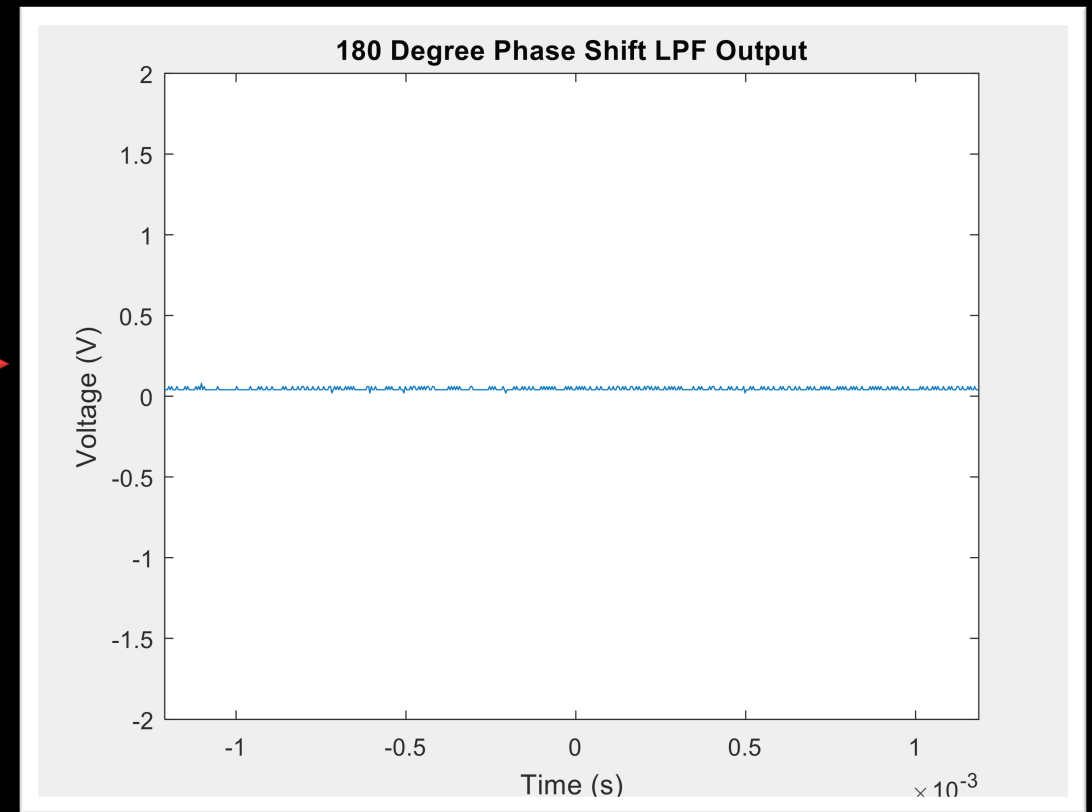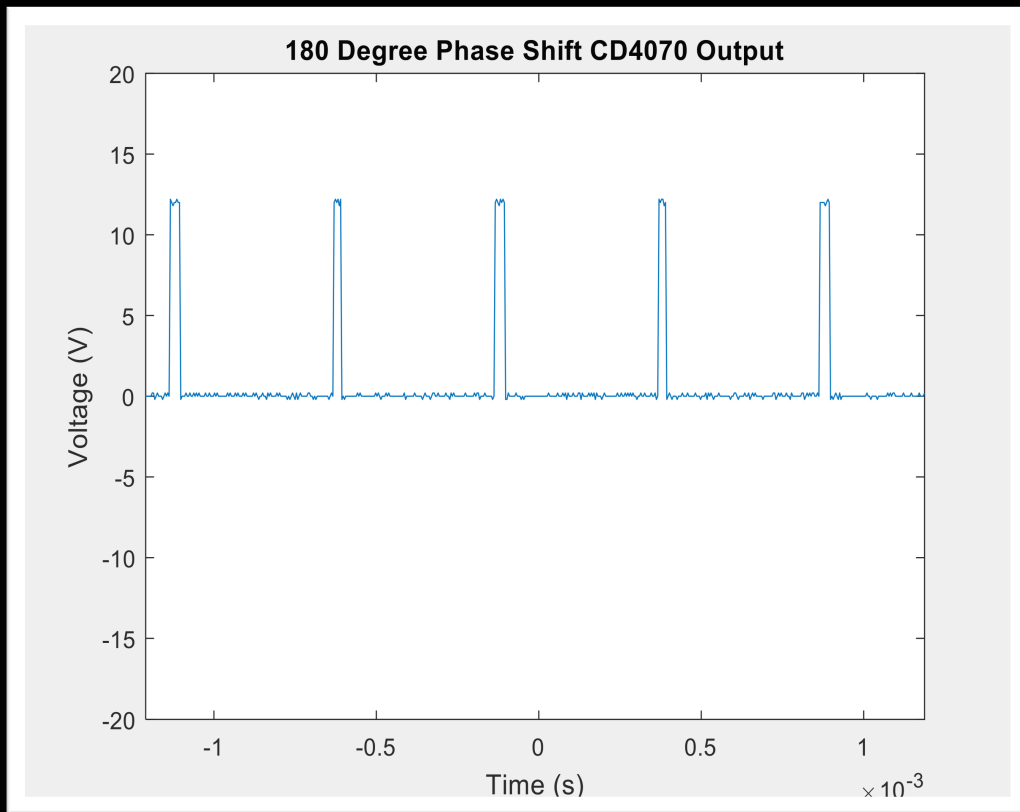






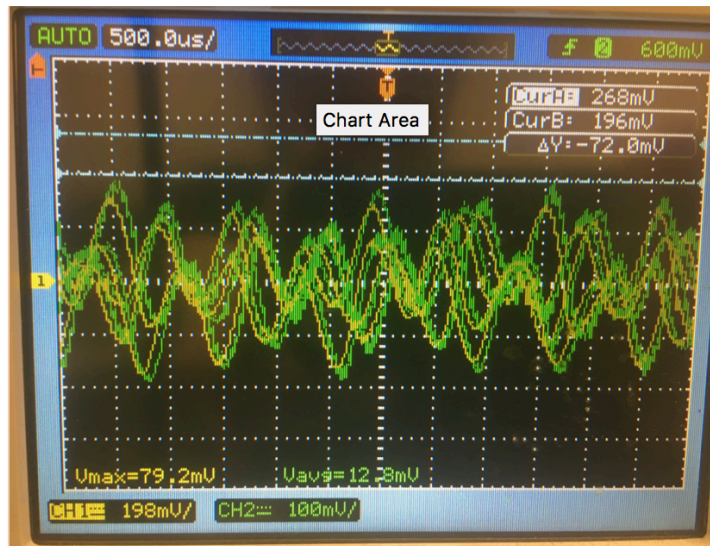
# CORRELATION OF COMPLICATED SIGNALS

Does work but results are less definitive due to high range of frequencies


Input Microphone Signals from Preamplifiers




Clipping Amplifier Outputs

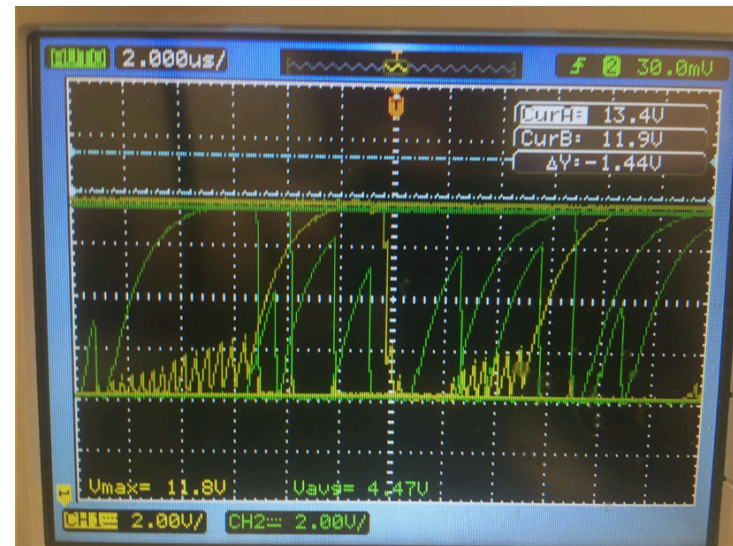


XOR Output

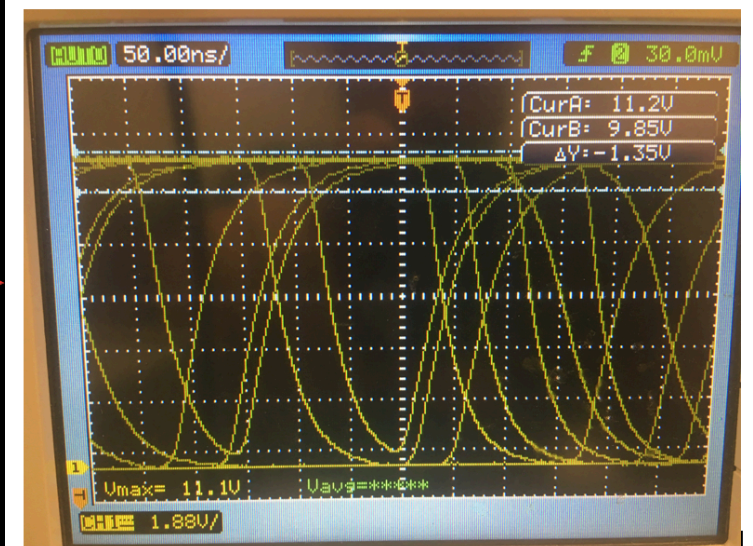

**LPF "In Phase" Output**

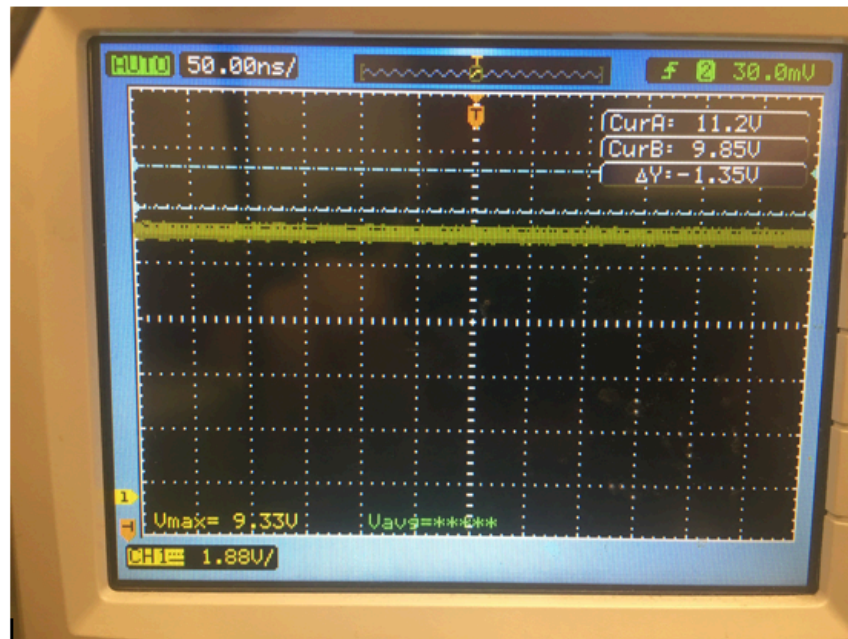

**LPF "Out of Phase" Output**

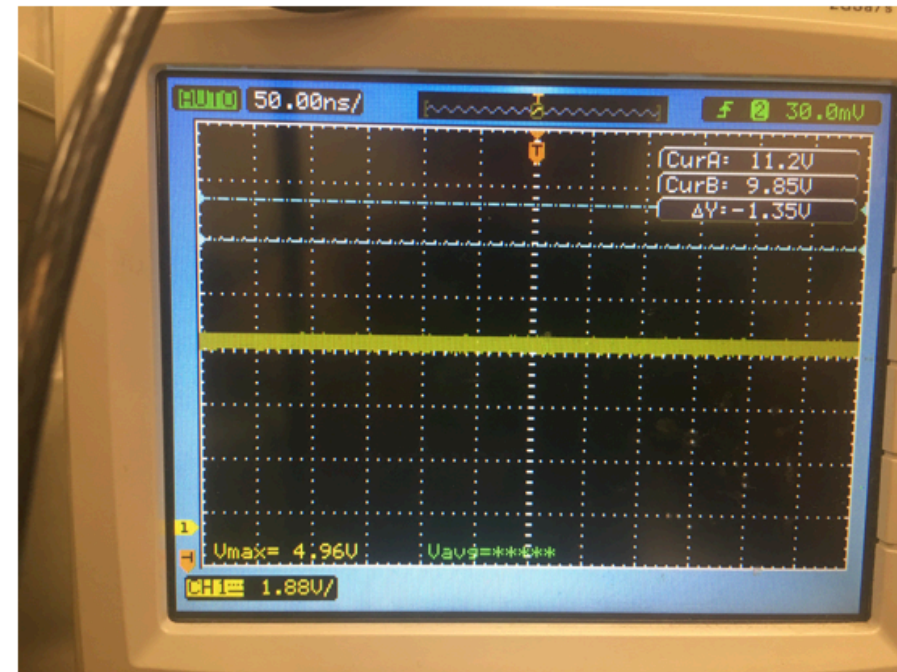





# FUTURE WORK

- Test with live instruments for recording purposes
- Implement all four correlators and test with 3 or more microphones
- Add a phase shifting option to allow user to manually change the phase of a desired signal
  - This would also require audio outputs



QUESTIONS?